

DEPARTMENT OF ELECTRONICS AGH UST

LABORATORY  
OF  
**ELECTRONIC ELEMENTS**

# Current Sources

REV. 1.0a

## 1. THE GOAL OF THE EXERCISE

The objective of the exercise is a practical verification of several types of current sources that are based on bipolar junction transistors.

## 2. THE UTILIZED MODELS AND ELEMENTS

During the exercise following components will be used:

- NI ELVIS Prototyping Board (ELVIS) connected with PC,
- Virtual measurement devices:
  - Two-Wire Current-Voltage Analyzer (2-Wire)
  - Digital Multimeter (DMM),
  - Variable Power Supplies (VPS)
- Set of electronic elements listed in Table 1.

Table 1. Values of electronic elements required to perform the exercise

Resistors	2x2k $\Omega$ , 4.7k $\Omega$ , 6.2k $\Omega$ , 11k $\Omega$ , 43k $\Omega$ , 62k $\Omega$
Transistors	4xBFP519

## 3. PREPARING THE DRAFT

3.1. Look at datasheets, identify, and draw the footprint with terminals for bipolar junction transistor BFP519.

3.2. Try to analyse in a qualitative way the current source shown in Figure 3.1.

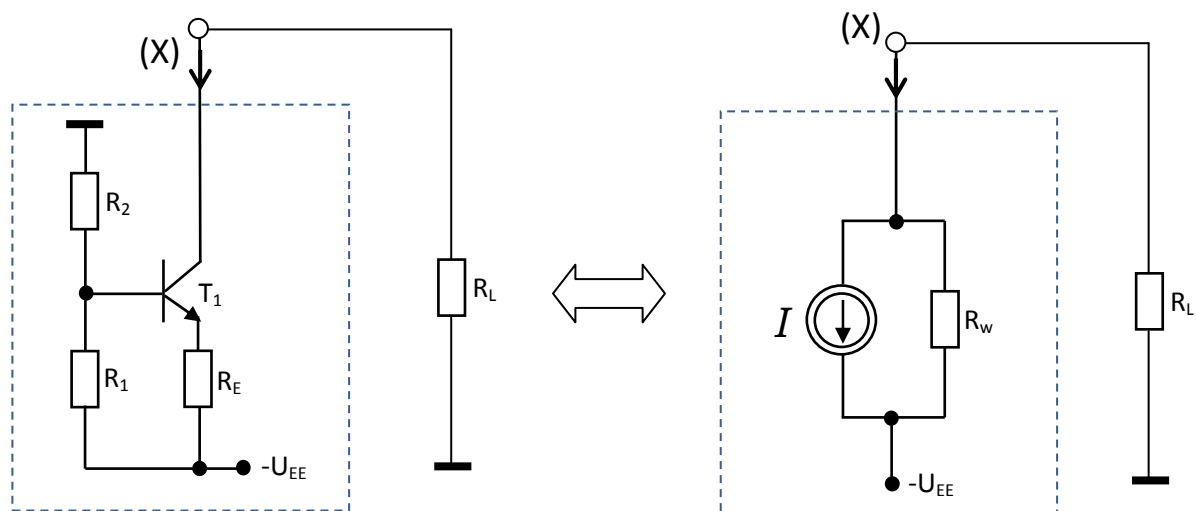


Fig. 3.1. Basic current source based on one bipolar junction transistor.

- 3.3. Try to deduce the formula (3.1), describing the value of the current source  $I$ . When deriving the formula skip the importance of the transistor base current.


$$I = \frac{U_{EE} \frac{R_1}{R_1 + R_2} - U_{BE}}{R_E} \quad (3.1)$$

- 3.4. \* Try to deduce the formula (3.2), describing the value of the internal resistance  $R_w$  of the current source. Instead of the transistor, one should use its small-signal equivalent model ( $R_B = R_1 || R_2$ ).

$$R_w = R_E || (r_{be} + R_B) + r_{ce} \left( 1 + g_m \frac{R_E \cdot r_{be}}{R_E + r_{be} + R_B} \right) \quad (3.2)$$

\* - extra task

- 3.5. Try to deduce the formula (3.3), describing the value of the current  $I$  of the current mirror shown in Fig. 3.2. Note, that  $U_{BE1} = U_{BE2}$ , moreover transistor  $T_1$  works in a diode mode ( $U_{CE1} = U_{BE1}$ ).

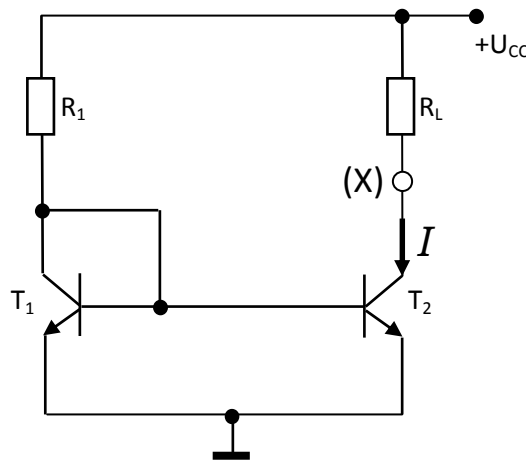


Rys. 3.2. Basic current mirror.

$$I = I_{C2} = \frac{U_{CC} - U_{BE1}}{R_1} \quad (3.3)$$

- 3.6. Try to deduce the formula (3.4), describing the value of the current  $I$  of the Wilson current mirror shown in Fig. 3.3. Note, that  $U_{CE1} = U_{BE1} + U_{BE2}$ .

$$I = I_{C3} = \frac{U_{CC} - 2U_{BE}}{R_1} \quad (3.4)$$

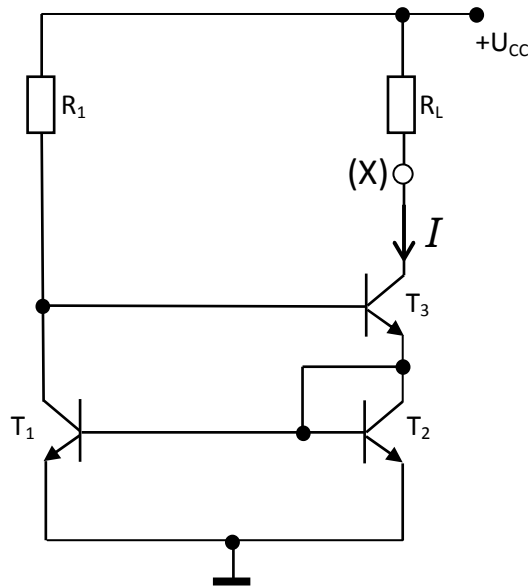

Rys. 3.3. Wilson current mirror.

## 4. THE COURSE OF THE EXERCISE

- 4.1. Connect the elements according to the scheme shown in Fig. 3.1:  $T_1 \rightarrow \text{BFP519}$ ,  $R_1 = 43\text{k}\Omega$ ,  $R_2 = 62\text{k}\Omega$ ,  $R_E = 2\text{k}\Omega$ ,  $-U_{EE} = -V_{PS} = -12\text{V}$ . Instead of resistor  $R_L$  (removed from the circuit), join DUT+ to point X, while GROUND join with DUT-. Launch the 2-Wire Analyzer, set the voltage range from 0 to +10V with a step +0,05V, set the current limit to +20mA. Under these settings, carry out measurements to get  $I=f(U)$  characteristic of the current source. Next, change the value of the resistor  $R_E$  to 4.7k $\Omega$ , after that to 11k $\Omega$ , and take the current source characteristics for these cases. Record the measurements using „log” option.
- 4.2. For the scheme from Fig. 3.1, with  $R_E = 2\text{k}\Omega$ , instead of 2-Wire Analyzer, connect the joined in series ammeter (DMM) and load resistor  $R_L = 2\text{k}\Omega$ , between X and the GROUND. Measure the current of the source. Next, change the  $R_L$  to 11k $\Omega$  and repeat the measurement.
- 4.3. Connect the elements according to the scheme shown in Fig. 3.2:  $T_1 \rightarrow \text{BFP519}$ ,  $R_1 = 11\text{k}\Omega$ ,  $+U_{CC} = +V_{PS} = +12\text{V}$ . Instead of resistor  $R_L$  (removed from the circuit), join DUT+ to point X, while the GROUND join with DUT-. Launch the 2-Wire Analyzer, set the voltage range from 0 to +12V with a step +0,05V, set the current limit to +20mA. Under these settings, carry out measurements to get  $I=f(U)$  characteristic of the current source. Next, change the value of the resistor  $R_1$  to 4.7k $\Omega$ , and repeat the measurements. Record the measurements using „log” option.
- 4.4. Connect the elements according to the scheme shown in Fig. 3.3:  $T_1 \rightarrow \text{BFP519}$ ,  $R_1 = 11\text{k}\Omega$ ,  $+U_{CC} = +V_{PS} = +12\text{V}$ . Instead of resistor  $R_L$  (removed from the circuit), join DUT+ to point X, while the GROUND join with DUT-. Launch the 2-Wire Analyzer, set the voltage range from 0 to +12V with a step +0,05V, set the current limit to +20mA. Under these settings, carry out measurements to get  $I=f(U)$  characteristic of the current source. Next, change the value of the resistor  $R_1$  to 4.7k $\Omega$ , and repeat the measurements. Record the measurements using „log” option.

## 5. DATA ANALYSIS

- 5.1. Draw characteristics  $I=f(U)$  of the current source, taking into account the measurements collected at point 4.1, for different values of the resistor  $R_E$ . Are the measured current values in line with the theoretical ones, according to the formula 3.1?
- for each case, try to estimate graphically the internal resistance  $R_w$  of the current source. Assuming that the Early' voltage of the transistor is  $U_A=200V$ ,  $\beta=100$ , find the small-signal parameters for  $R_E=2k\Omega$ , at operating point ( $U_{CE}=5V$ ,  $I_C=I$ ), and next estimate the theoretical value of  $R_w$  according to the formula 3.2,
  - how would the  $I=f(U)$  characteristic look like when extrapolated in the direction of negative voltages, that is, if we would change the voltage  $U$  from  $-10V$  to  $+10V$ , instead from  $0V$  to  $+10V$ . Consider this case only for  $R_E=2k\Omega$ .
- 5.2. Clarify, why you obtained different values of current at point 4.2, when  $R_L=2k\Omega$  and  $R_L=11k\Omega$  were used, respectively. Why does the current source is not working properly in the latter case? What is the threshold value of  $R_L$ , above which the source stops to deliver constant current?
- 5.3. Draw characteristics  $I=f(U)$  of the current source, taking into account the measurements collected at point 4.3, for different values of the resistor  $R_1$ . Are the measured current values in line with the theoretical ones, according to the formula 3.3?
- for each case, try to estimate graphically the internal resistance  $R_w$  of the current source,
  - what is the threshold value of  $R_L$ , above which the source stops to deliver constant current?
- 5.4. Draw characteristics  $I=f(U)$  of the current source taking into account the measurements collected at point 4.4, for different values of the resistor  $R_1$ . Are the measured current values in line with the theoretical ones, according to the formula 3.4?
- for each case, try to estimate graphically the internal resistance  $R_w$  of the current source,
  - what is the threshold value of  $R_L$ , above which the source stops to deliver constant current.
- 5.5. Try to compare and comment the graphically estimated values of  $R_w$  for different current sources subjected to measurements during this exercise.

## 6. LITERATURE

- [1] Lecture (P. Dziurdzia)
- [2] Behzad Razavi „Fundamentals of Microelectronics”
- [3] S. Kuta, „Elektronika” Part 1