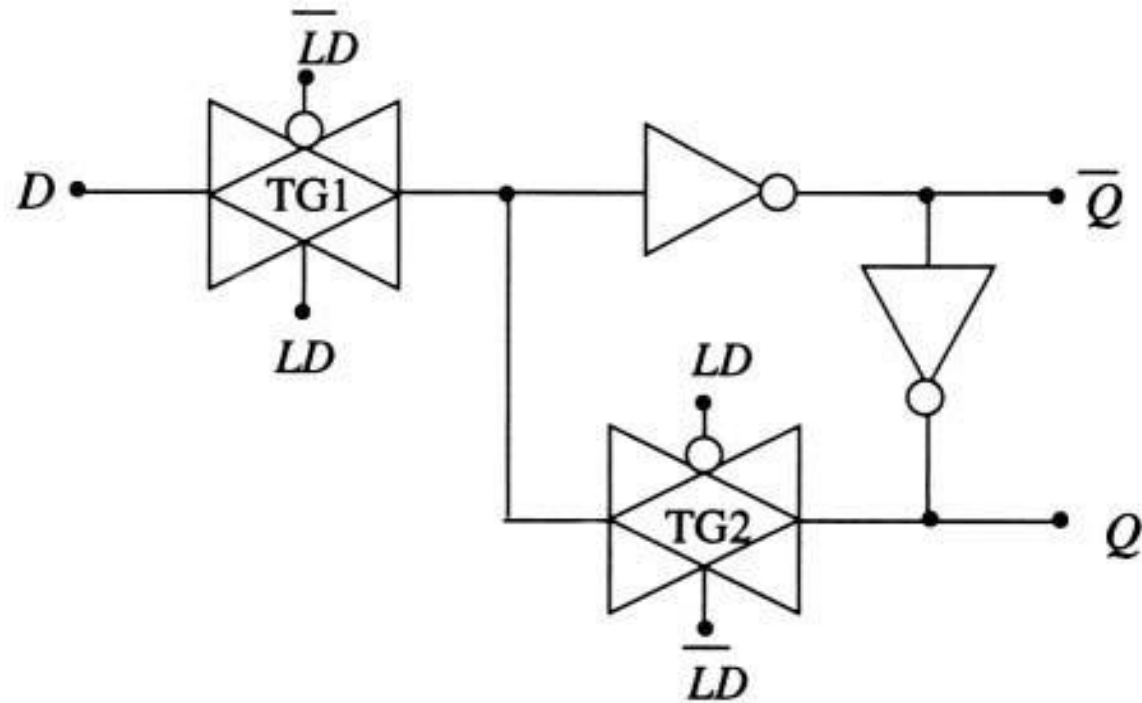


Digital CMOS circuits

D flip-flop

D-latch based on transmission gate


D-latch



Why are transmission gates needed in the latch?

D-latch – work

If there were no transmission gates:

 


It works as the latch!

Is there any problem?

What about with input?

D-latch – work

 If there were no transmission gates – driving




What will be the logical state here?

Symmetrical inverters


D-latch – work

 If there were no transmission gates – driving



D-latch – work

 
If there were no transmission gates – driving




Symmetrical inverters

**Two NOT gates it is not enough,
switches are needed – transmission gates.**

D-latch – work

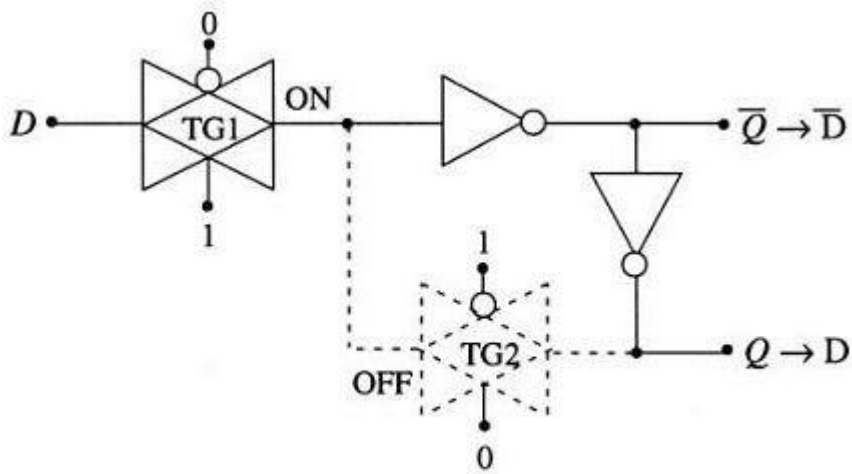


(a) Load operation with $LD=1$

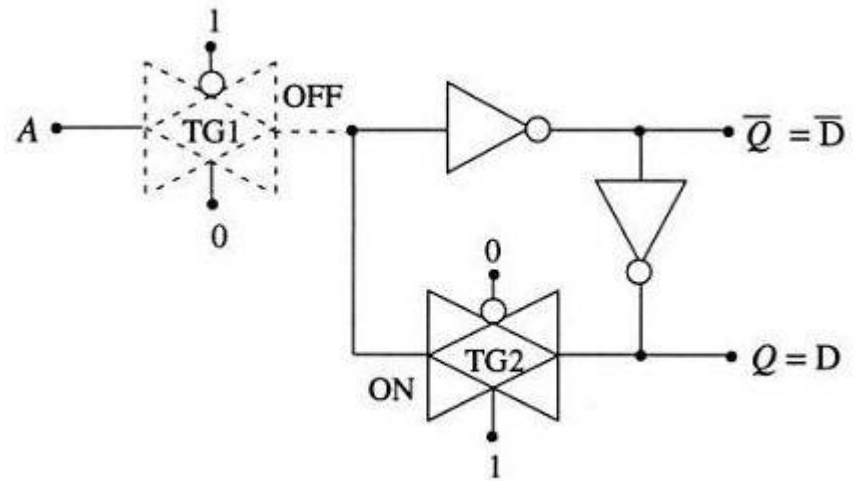


(b) Hold operation with $LD=0$

D flip-flop – schematic

 


D flip-flop – work

$\phi = 0, \bar{\phi} = 1$ – load

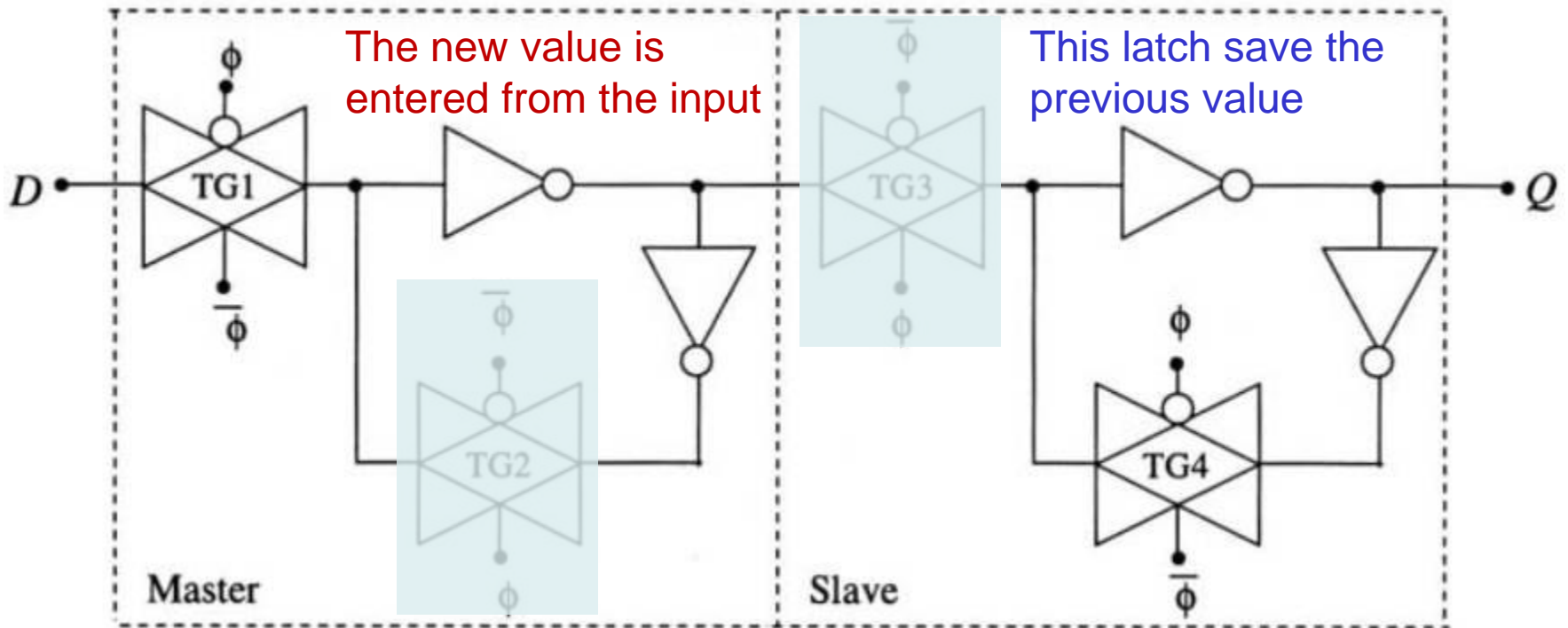


D flip-flop – work

$\phi = 1, \bar{\phi} = 0$ – latching

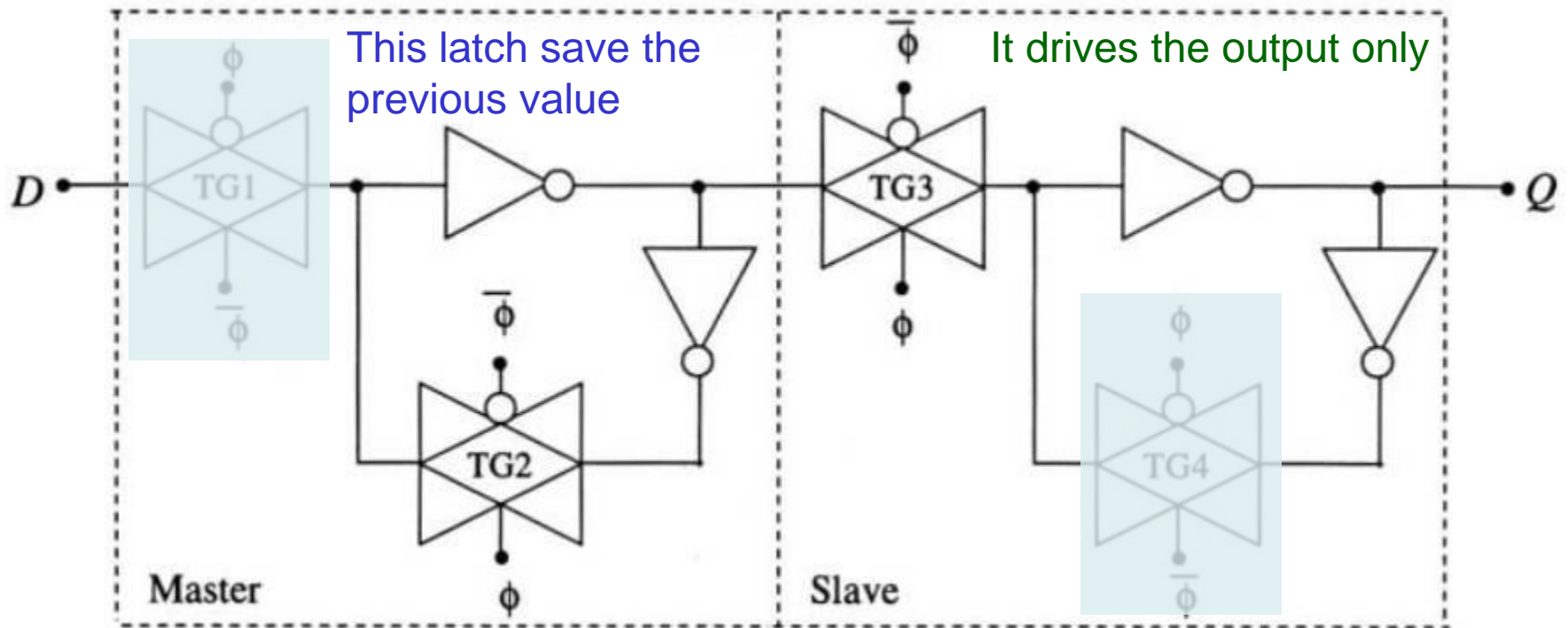


Layout drawing – the stick diagram

schematic → layout

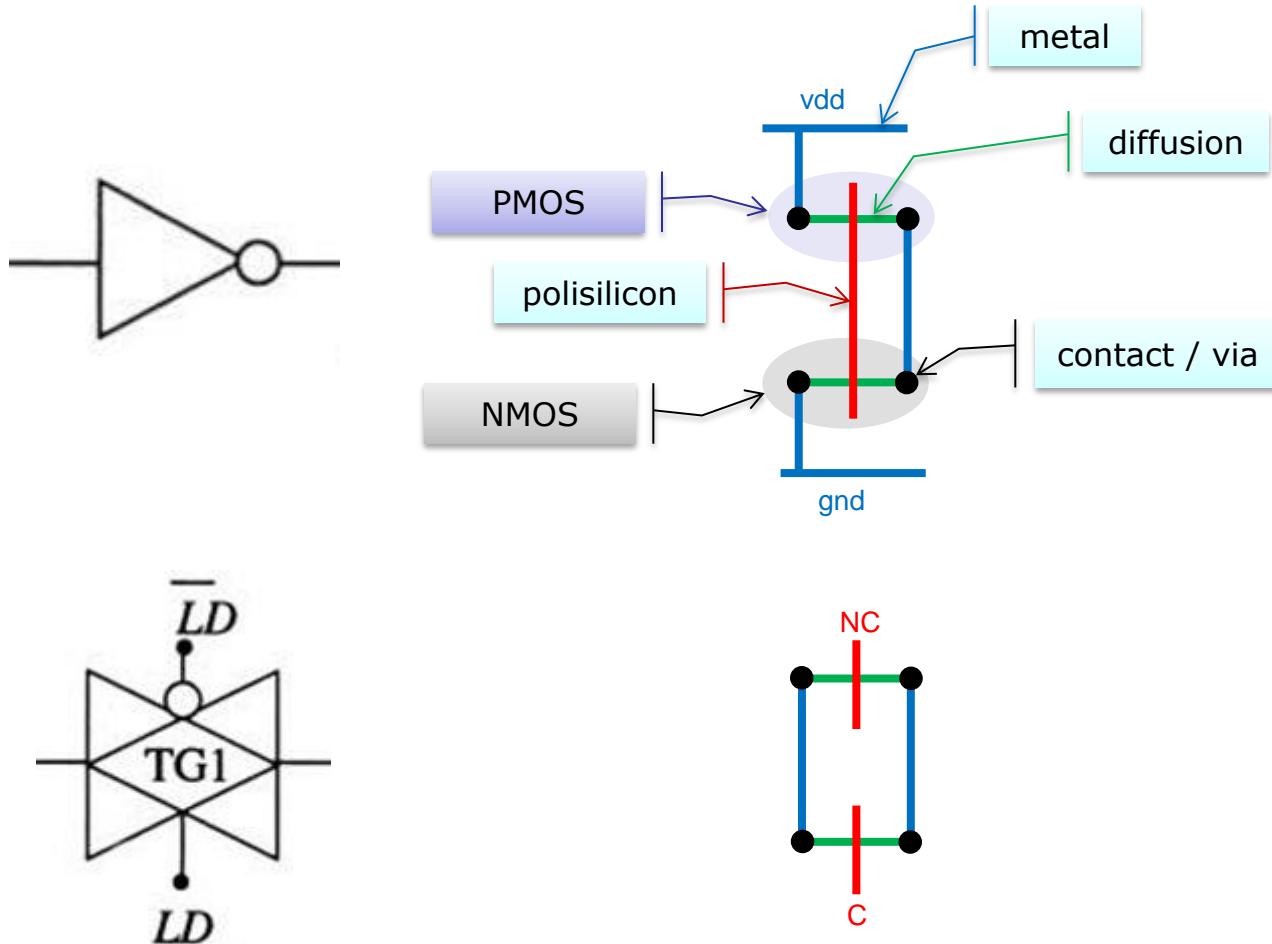


D flip-flop

schematic → layout

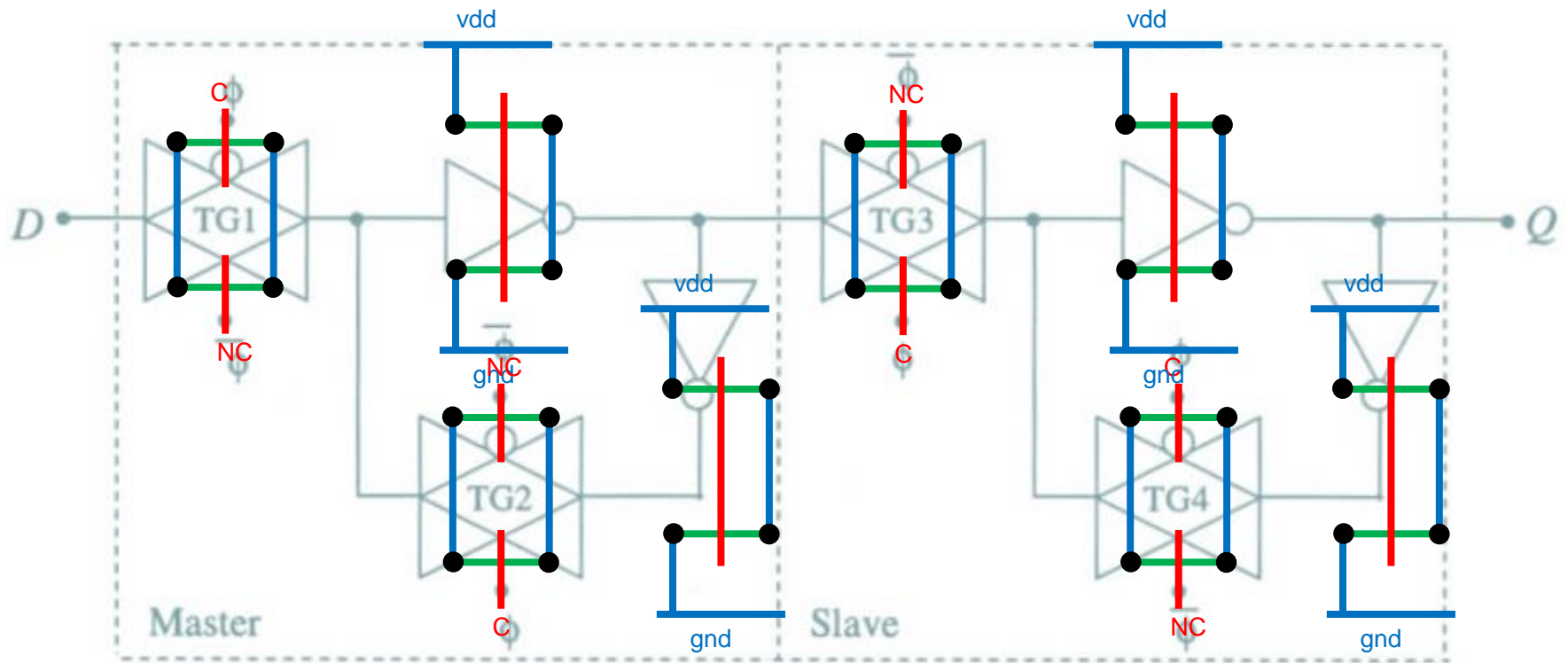

D flip-flop

schematic → layout

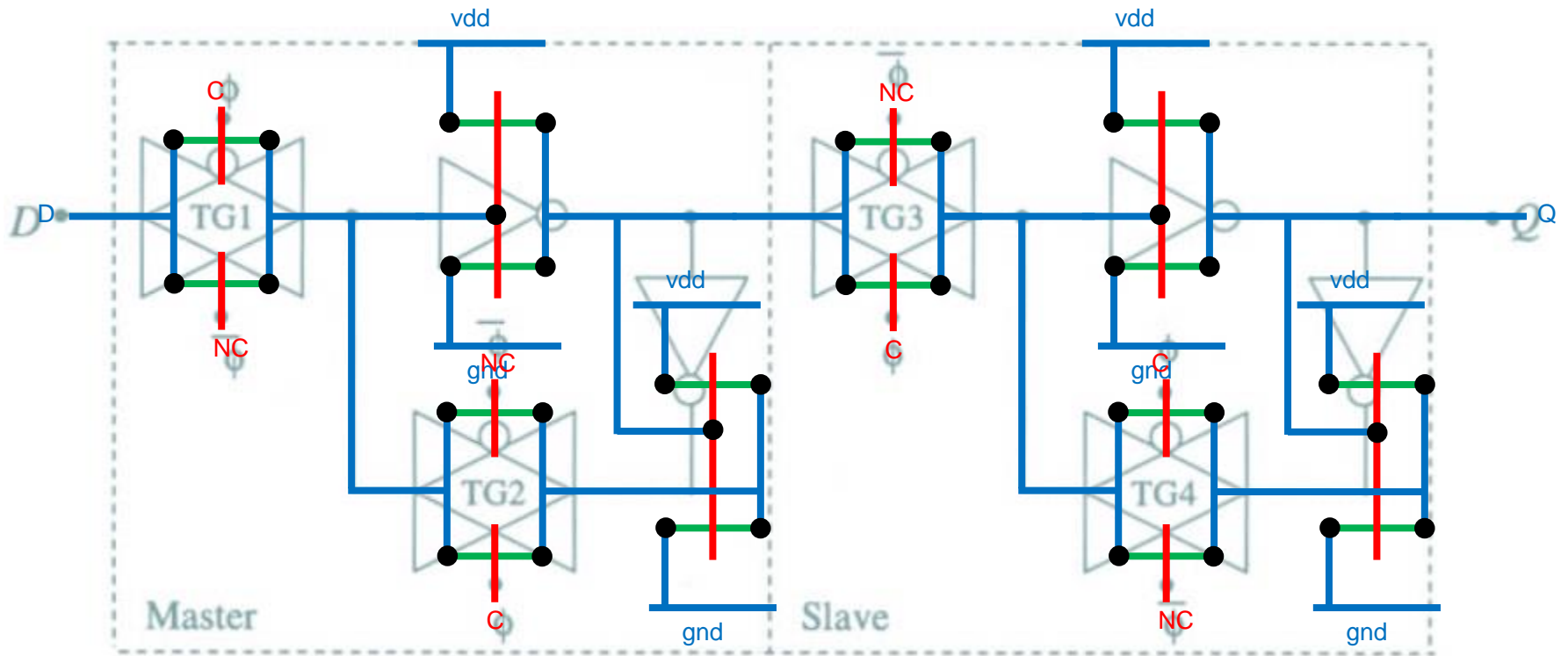




AGH

D flip-flop

The layout optimisation (1st latch)

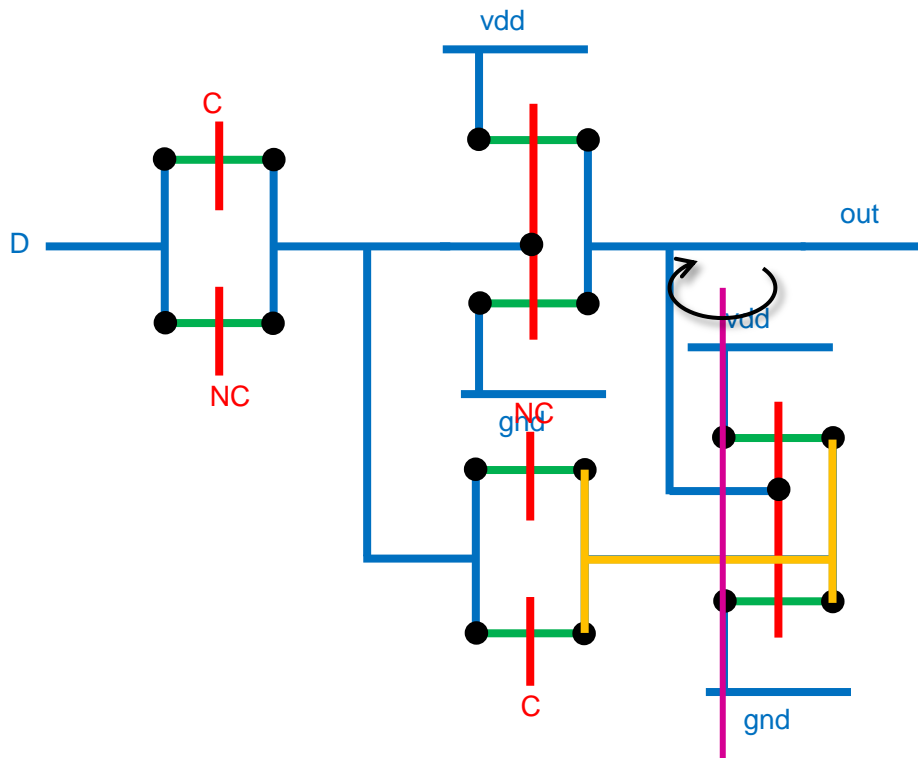




AGH

D flip-flop

The layout optimisation (1st latch)

 




AGH


D flip-flop

The layout optimisation (1st latch)

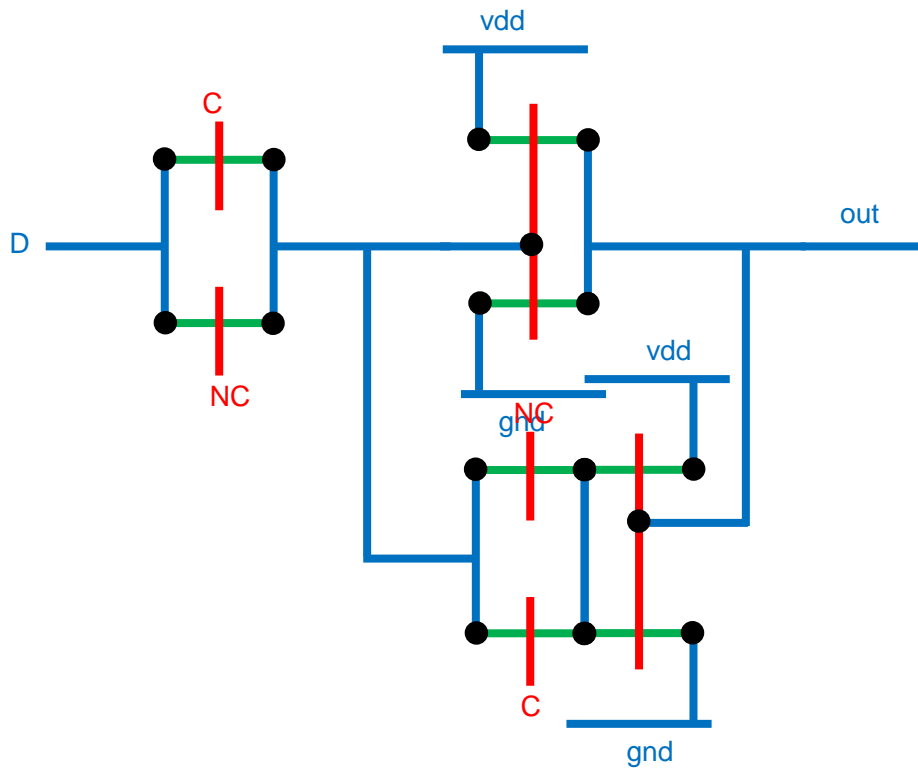


D flip-flop

The layout optimisation (1st latch)

 

D flip-flop

The layout optimisation (1st latch)


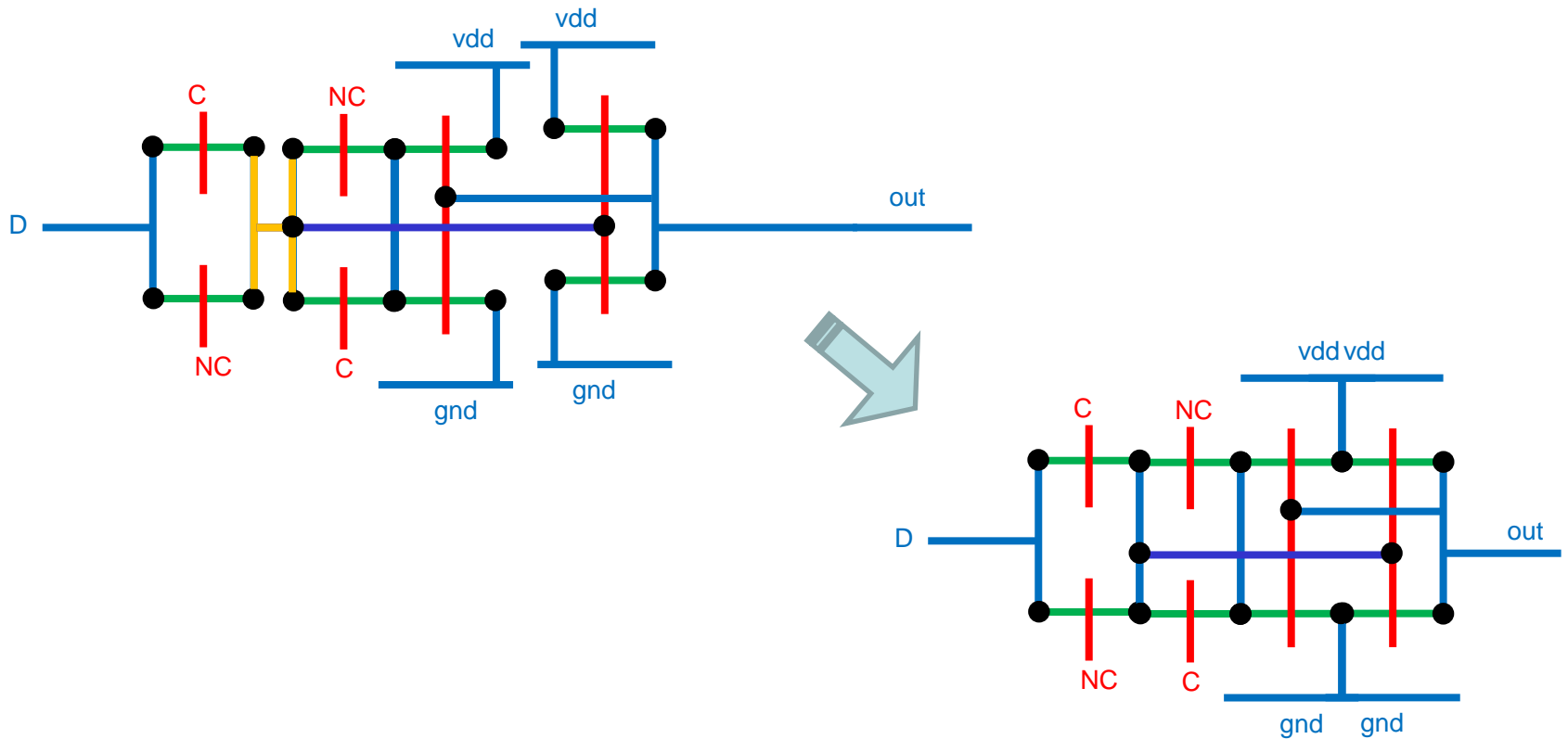




AGH

D flip-flop

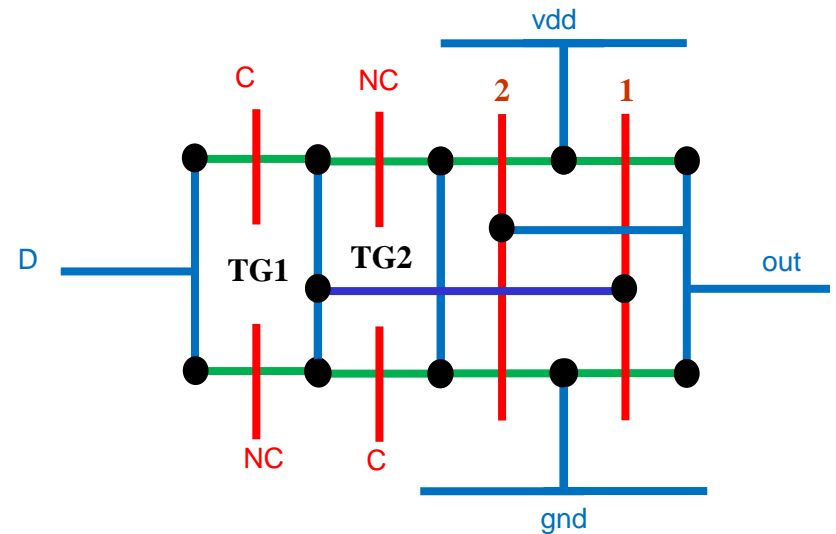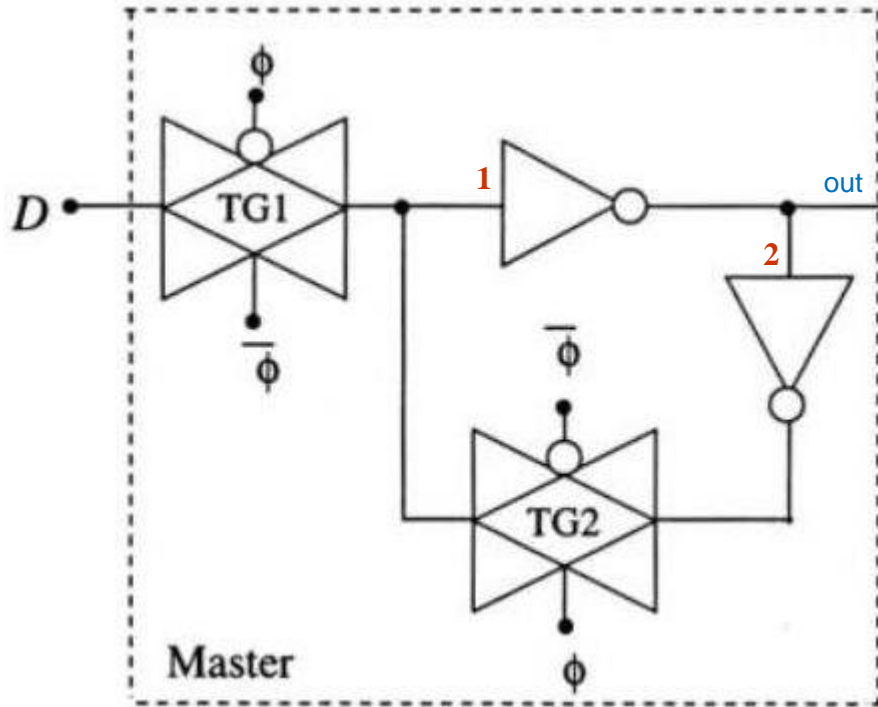The layout (1st latch) – comparison with the schematic





AGH

D flip-flop

The optimised layout

