

Laboratory of Integrated Systems Design

Department of Electronics

AGH University of Science and Technology in Cracow

Task 6

Design of a buffer with large load transistors with big dimensions

1. Purpose

Familiarizing students with designing of have load buffer and calculations. Optimisation of a layout with big dimensions transistors (multi-finger transistors).

2. Task

- Perform simulations and measure propagation times (t_{pHL} , t_{pLH}) for a symmetrical inverter (see section 4.1) with the minimum dimensions for the load capacitance chosen from Tab. 1.
- Based on the theory [1] calculate number of the buffer stages (N) and size factor (A) assuming input capacitance $C_{IN} = 3,5\text{fF}$.
- Draw a circuit diagram for the above mentioned calculations. Perform a simulation confirming the correct work of the buffer and measure the its propagation times. Check how the increase in the size factor A (and the decrease in the number of stages N) will affect the propagation times. You can try to increase A one and a half times or twice.
- Draw a buffer layout using multi-finger transistors. Choose the size of the fingers so that the transistor "heights" are the same and they could be easy connected together. Pay attention to minimizing the area of the layout.
- Extract the netlist from the layout with parasitic parameters: R and C. Perform post-layout simulations to measure timing parameters (propagation times, rise and fall times) when loading the buffer with given capacitance. And measure average power consumption of the buffer without load.

3. Result

- Present the final layout to check by the teacher.
- Write a short report containing: the goal of the project and the results of pre-layout and post-layout simulations – compare times values when the given capacitance is driven by minimum inverter and the designed buffer. Collect (in a table) parameters of the buffer: i.e.: timing parameters, average power consumption, dimensions and area. Please remember to give the conditions the gate simulations (load capacitance, signal frequency, etc.). It is not advisable to place the topography in the report, but it is necessary to specify the path and name of the library where the final version of the project exist in your account. The report can be sent by e-mail, entering the subject of the letter: ICS_task6_name_surname.

Table 1. Load capacitance values for the buffor [pF].

L.p.	1	2	3	4	5	6	7	8
C_{load}	0.2	0.5	1	3	5	10	25	50

4. References

1. R. Jacob Baker, CMOS: Circuit Design, Layout, and Simulation, 3rd Edition, October 2010, Wiley-IEEE Press, pp. 344 - 346.

5. Realization of the task – useful information

5.1. Schematic

The goal of the project is to minimize propagation times, thus, the minimum dimensions of transistors in the inverter for which we obtain the same propagation times t_{pLH} and t_{pHL} are: $WP = 720$ nm and $WN = 240$ nm with the length $L = 180$ nm (Task 1). The input capacity of such an inverter is approx. $3fF$.

Drawing the schematic you should choose the size of fingers of the transistors in such way that, in subsequent stages (transistors) it is the same, and increase only the number of fingers to obtain assumed total width of the transistor. When drawing the schematic, enter the total width and number of fingers or finger dimension for each transistor, and the program will calculate the number of fingers (see Fig.1 below).

The screenshot shows the 'Edit Object Properties' dialog box. The 'CDF Parameter' section is highlighted with a red box. The parameters are as follows:

Property	Value	Display
Library Name	UMC_18_CMOS	off
Cell Name	N_18_NM	off
View Name	symbol	off
Instance Name	M0	off
CDF Parameter		
Model Name	n_18_nm	off
Total Width	720.0n M	off
Finger Width	240.0n M	off
Length	180.0n M	off
Finger Number	3	off
mis_flag	1	off
Source Drain Metal Width	400.0n M	off
AD AS PD PS Editable	<input type="checkbox"/>	off
Drain diffusion area (m ²)	1.578667e-13	off
Source diffusion area (m ²)	1.578667e-13	off
Drain diffusion periphery	1.413333u M	off
Source diffusion periphery	1.413333u M	off
Multiplier	1	off

Fig. 1. Window for editing of a transistor parameters

5.1. Layout

The best way is to generate the layout automatically, next arrange transistors and connect them. Since the fingers of all transistors should to have the same dimension, the transistors visible on the topography will have the same vertical dimension and different horizontal, so they can be arranged side by side. All you need to do is connect the drains, sources and gates.

Below, in Figure 2, exemplary layout of transistors with identical finger sizes are shown. As you can see, the multi-finger transistor consists of several transistors that can be connected in parallel.

On one of them, metal layers have been marked, which have to be connected in order to create a drain and source of the transistor. The polysilicon strips should also be drawn to create the gate.

 


Fig. 2. Exemplary layouts of multi-finger transistors

Drawing the layout parameters of a transistor can be modified (Fig. 3).

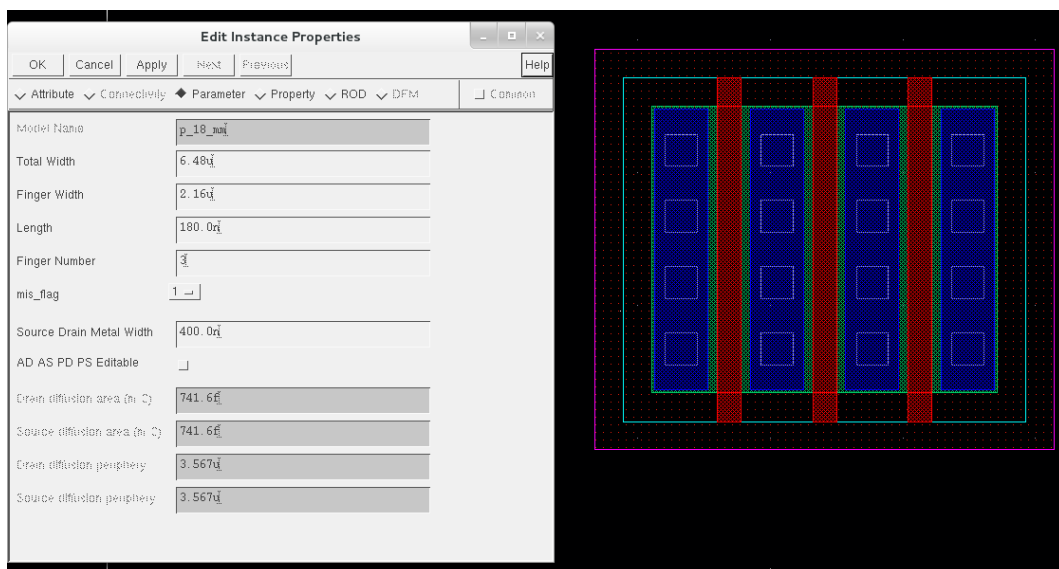


Fig. 3. Window for editing of transistor parameters in Virtuoso Layout Editor